



Date: / / 2017  
Time: 3 hours  
Examiner: *Enas Tariq*

Second Trial  
2016-2017

Subject: Logic Design  
Class: 1<sup>st</sup>

Note: Answer six questions.

Q1/ Answer two only

- a) Prove  $X + 1 = 1$ ?  
b) Simplify the following using Demorgan theorem:  
$$Y = ABCD + ABCD + ABCD + ABCD + ABCD + ABCD + ABCD$$

c) Simplify the following Boolean expression:

$$Y = \overline{AB} + \overline{AC} + \overline{A} \overline{BC}$$

Q2/ Simplify using Karnaugh map of the following function: (Choose One)

- 1)  $F(A, B, C, D) = AB + ABC + ABCD + ACD + ABCD$   
2)  $F(A, B, C, D) = \overline{A} \overline{B} \overline{C} + \overline{A} B + A B \overline{C} + AC$

Q3/ Answer the following: (Choose two only)

a) Using NAND gates only to implement the function:

$$F(A, B) = AB + (A + C)(B + C)$$

b) Determine the truth table and logic diagram of the function:

$$F(X, Y, Z) = X + \overline{Y}Z + Y\overline{Z}$$

Q4/ Design one of the following:

- a) Two 2\*4 decoders with enable inputs connected to form a 3\*8 decoder.  
b) Binary-to-octal line decoder or design 3-to-8 lines decoder.

Q5/ Answer the following: (Choose two)

- a) Implement 4-bit synchronous up counter.  
b) Design J. K. flip-flop.  
c) Design 4-to-1 line multiplexer with truth table.

Q6/ Answer the following:

- a) Design Full Adder using Half Adders with truth table.  
b) Design 4-bit shift register, and write wave, when the input is 10001.

Q7/ Draw the 4-bit parallel adder, find the sum and output carry for the addition of the following two 4 bit numbers if the input carry ( $C_{n-1}$ ) is 0:

$$A_4A_3A_2A_1 = 1110, B_4B_3B_2B_1 = 1010$$