




Subject : Electrical circuits
Branch : Applied physics
Examiner : Odai N Salman

Class : 2nd class
Time : 3 hours
Date :

Note: answer four questions only.


- Q1: For the network in Fig. 1:
- Determine the voltage V_{ab} using use Kirchoff's voltage law.
 - Calculate the current I .

Fig.1

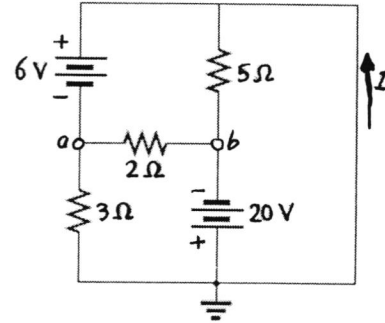


- Q2: : Using the principle of superposition, find the current I_2 through the 12 kΩ resistor in Fig. 2.

Fig.2

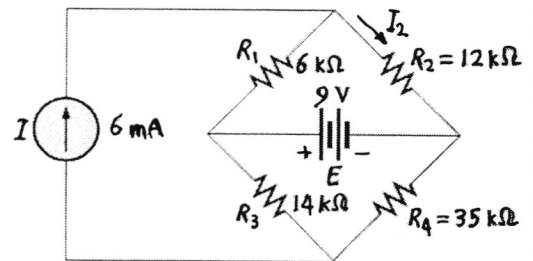


- Q3: Find the Thévenin equivalent circuit for the network external to the resistor R in each of the networks in Fig. 3.

Fig.3

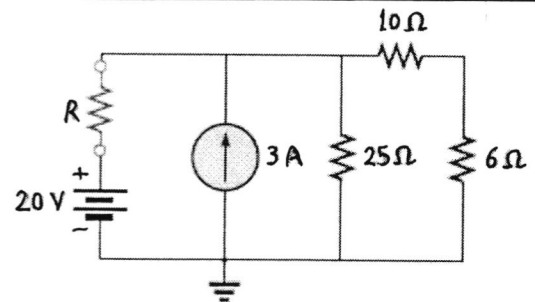

- Q4: a. Determine the nodal Voltages for the network in Fig. 4.
b. Find the voltage across each current source.

Fig.4

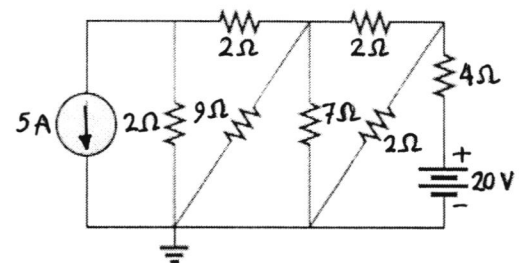

- Q5: Using mesh analysis, determine the currents for the network in Fig.5

Fig.5

