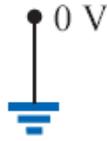


Voltage Sources and Ground


The symbol for the ground connection appears in Fig.(1) with its defined



Fig(1)

Ground potential

if we take the circuit of fig (2)

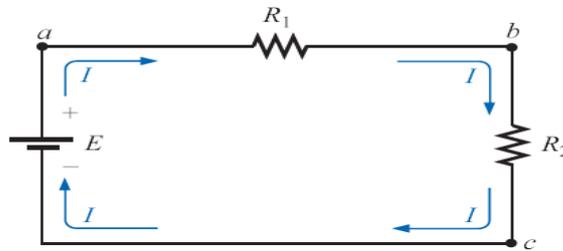

Fig(2)

If Fig.(2)is redrawn with a grounded supply, it might appear as shown in Fig. 3(a), (b), or (c). In any case, it is understood that the negative terminal of the battery and the bottom of the resistor R_2 are at ground potential.

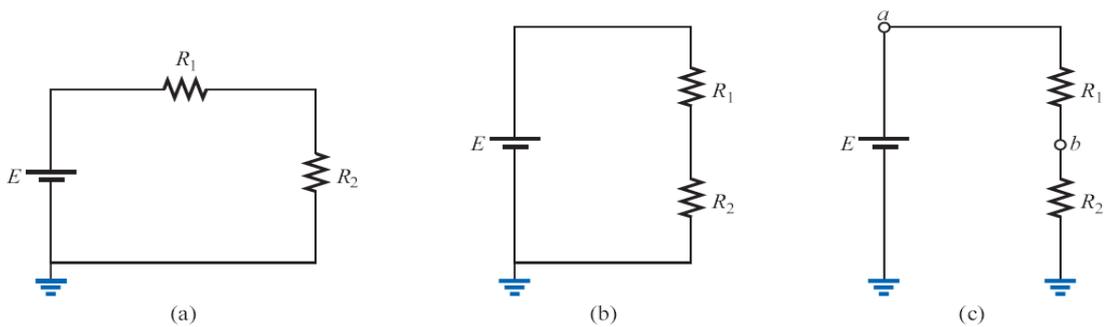


Fig (3)(a,b,c)

Three ways to sketch the same series dc circuit.

Example 1 Design a circuit by using the voltage divider rule of fig (4) such that ($V_{R1} = 4V_{R2}$).

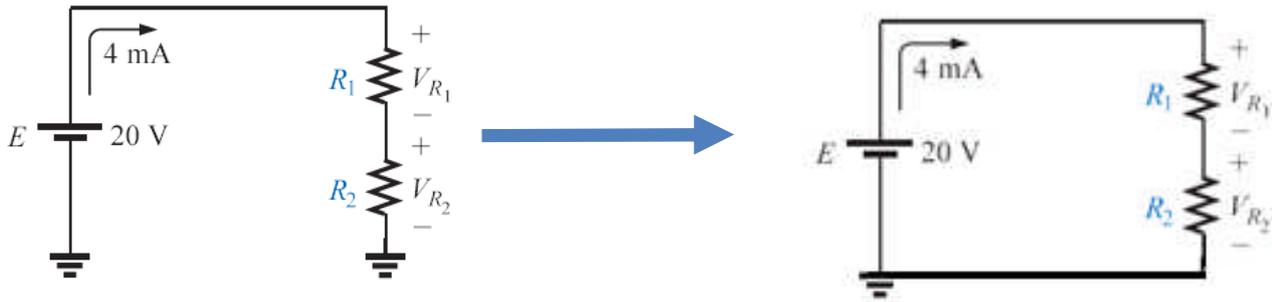


Fig.(4)

Solution: The total resistance is defined by :

$$R_T = \frac{E}{I} = \frac{20 \text{ V}}{4 \text{ mA}} = 5 \text{ k}\Omega$$

Since $V_{R_1} = 4V_{R_2}$,

$$R_1 = 4R_2$$

Thus $R_T = R_1 + R_2 = 4R_2 + R_2 = 5R_2$

and $5R_2 = 5 \text{ k}\Omega$
 $R_2 = 1 \text{ k}\Omega$

and $R_1 = 4R_2 = 4 \text{ k}\Omega$

Voltage sources may be indicated as shown in Figs. 5(a) and 6(a) rather than as illustrated in Fig. 5(b) and 6(b)..


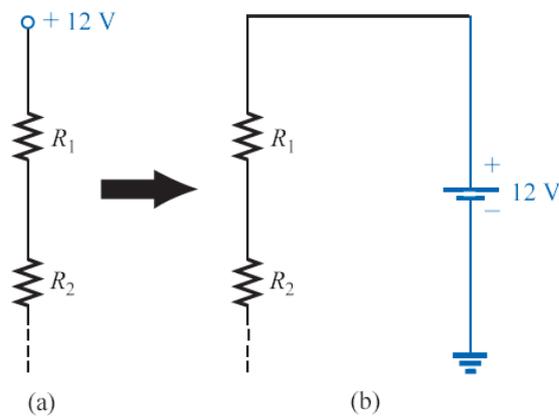


Fig (5)

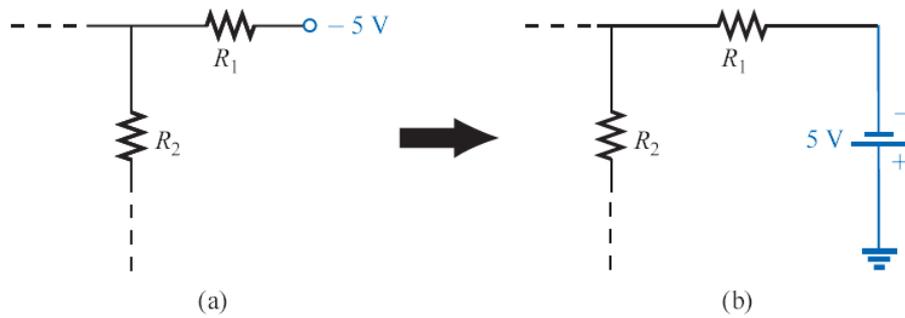Replacing the special notation for a positive dc voltage source with the standard symbol



Fig(6)


Replacing the notation for a negative dc supply with the standard symbol.

Double-Subscript Notation

The double-subscript notation V_{ab} specifies point (a) as the higher potential. If this is not the case, negative sign must be associated with the magnitude of V_{ab} .

In other words,

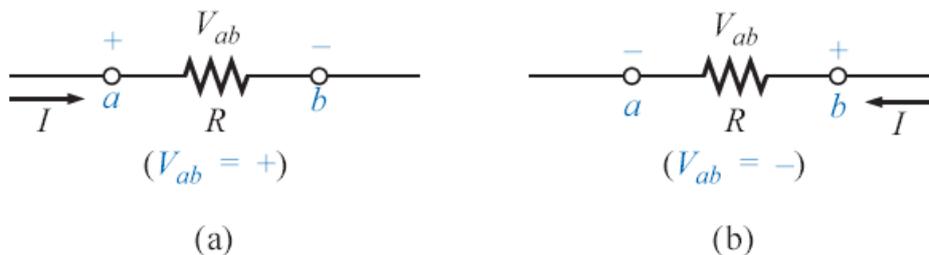the voltage V_{ab} is the voltage at point(a) **with respect to (w.r.t.)** point (b).



Fig(7)

The fact that voltage is an across variable and exists between two points has resulted in a double-subscript notation that defines the first subscript as the higher potential. In Fig. 7(a), the two points that define the voltage across the resistor R are denoted by (a and b). Since (a) is the first subscript for V_{ab} , point (a) must have a higher potential than point (b) if V_{ab} is to have a positive value. If, point (b) is at a higher potential than point (a), V_{ab} will have a negative value, as indicated in Fig. 7(b).

Single-Subscript Notation

The single-subscript notation (V_a) specifies the voltage at point a with respect to ground (zero volts).

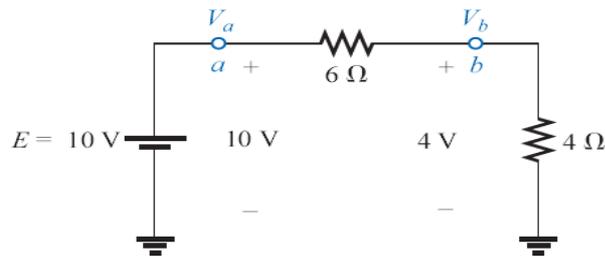


Fig.(8)

Defining the use of single-subscript notation

In Fig. 8, V_a is the voltage from point (a) to ground. In this case it is obviously 10 V since it is right across the source voltage E . The voltage V_b is the voltage from point (b) to ground. Because it is directly across the 4Ω resistor, $V_b = 4\text{ V}$.


the following relationship exists:

$$V_{ab} = V_a - V_b \quad (1)$$

So from the equation (1):

$$\begin{aligned} V_{ab} &= V_a - V_b = 10\text{ V} - 4\text{ V} \\ &= 6\text{ V} \end{aligned}$$

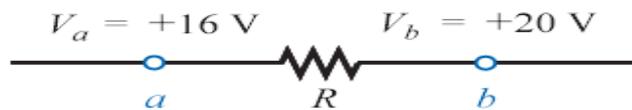EXAMPLE 2 Find the voltage V_{ab} for the conditions of Fig.(9)



Fig(9)


Solution: Applying Eq.(1)

$$\begin{aligned} V_{ab} &= V_a - V_b = 16\text{ V} - 20\text{ V} \\ &= -4\text{ V} \end{aligned}$$

☺ **Note:** the negative sign means that point (b) is at a higher potential than point (a).

EXAMPLE 3 Find the voltage V_a for the configuration of Fig.(10)

Solution: Applying Eq. (1):

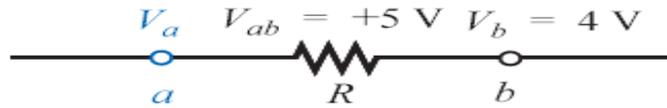

Fig(10)

$$V_{ab} = V_a - V_b$$

$$\text{and } V_a = V_{ab} + V_b = 5 \text{ V} + 4 \text{ V}$$

$$= 9 \text{ V}$$

EXAMPLE 4 Find the voltage V_{ab} for the configuration of Fig.(11)

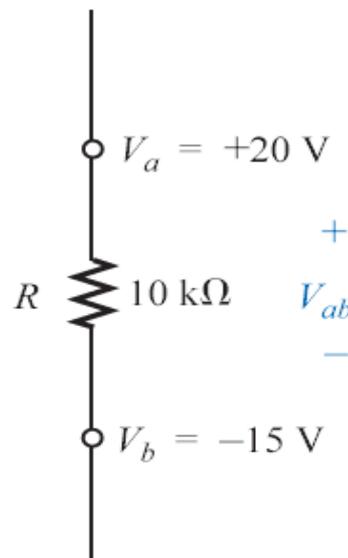


Fig (11)

Solution: Applying Eq. (1):

$$V_{ab} = V_a - V_b = 20 \text{ V} - (-15 \text{ V}) = 20 \text{ V} + 15 \text{ V}$$

$$= 35 \text{ V}$$

EXAMPLE 5 Find the voltages V_b , V_c , and V_{ac} for the network of Fig(12).

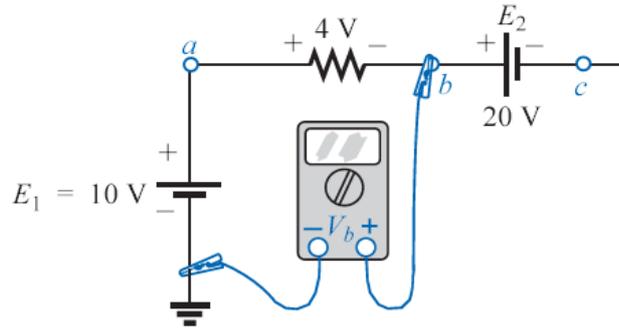


Fig (12)


Solution: Starting at ground potential (zero volts), we proceed through a rise of 10 V to reach point (a) and then pass through(a) drop in potential of 4 V to point (b). The result is that the meter will read :

$$V_b = +10 \text{ V} - 4 \text{ V} = 6 \text{ V}$$


$$V_c = V_b - 20 \text{ V} = 6 \text{ V} - 20 \text{ V} = -14 \text{ V}$$

$$\begin{aligned} V_{ac} &= V_a - V_c = 10 \text{ V} - (-14 \text{ V}) \\ &= 24 \text{ V} \end{aligned}$$

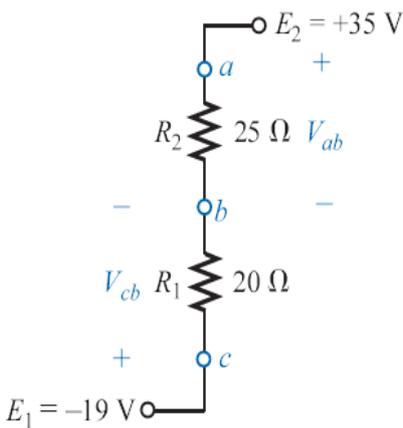
EXAMPLE 6 Determine V_{ab} , V_{cb} , and V_c for the network of Fig.(13)



Fig(13)

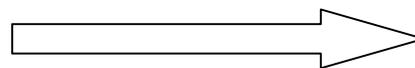

Redraw the network as shown in Fig. (14)

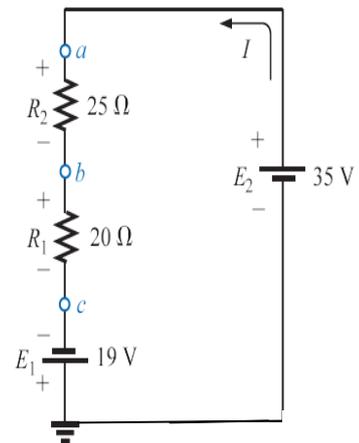

Fig(14)

$$E_T = 19 + 35 = 54 \text{ V}$$

$$R_T = 20 + 25 = 45$$


Sol: $I = \frac{54 \text{ V}}{45 \Omega} = 1.2 \text{ A}$

$V_{ab} = IR_2 = (1.2 \text{ A})(25 \Omega) = 30 \text{ V}$


$V_{cb} = -IR_1 = -(1.2 \text{ A})(20 \Omega) = -24 \text{ V}$

$V_c = E_1 = -19 \text{ V}$

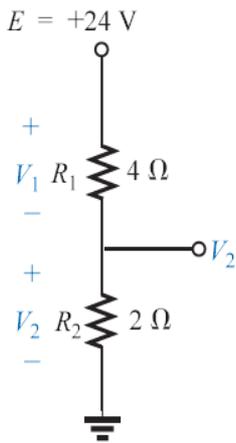EXAMPLE 7 Using the voltage divider rule, determine the voltages V_1 and V_2 of Fig.(15).



Fig(15)

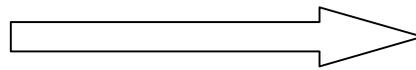

Redraw the network as shown in Fig. (16)


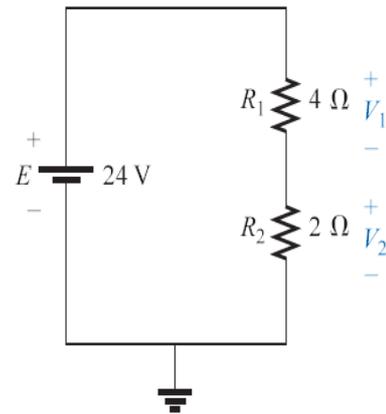


fig (16)


$$V_1 = \frac{R_1 E}{R_1 + R_2} = \frac{(4 \Omega)(24 \text{ V})}{4 \Omega + 2 \Omega} = 16 \text{ V}$$

$$V_2 = \frac{R_2 E}{R_1 + R_2} = \frac{(2 \Omega)(24 \text{ V})}{4 \Omega + 2 \Omega} = 8 \text{ V}$$


EXAMPLE 8 For the network of Fig. (17)

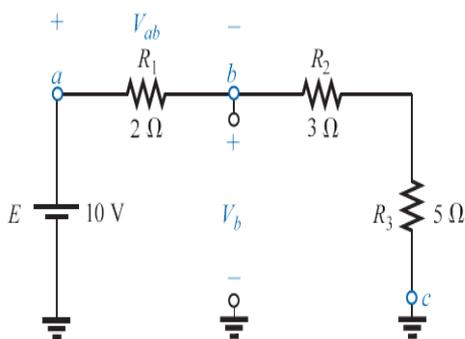

a

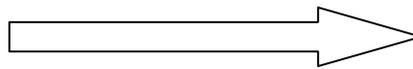

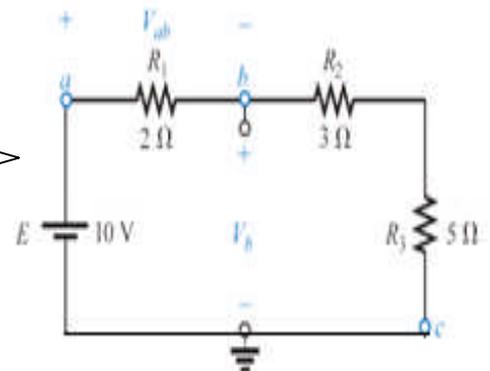Redraw the network as shown in Fig. (17 b)



b

Fig(17)

- Calculate V_{ab} .
- Determine V_b .
- Calculate V_c .

Solutions:

- Voltage divider rule:

$$V_{ab} = \frac{R_1 E}{R_T} = \frac{(2 \Omega)(10 \text{ V})}{2 \Omega + 3 \Omega + 5 \Omega} = +2 \text{ V}$$

- Voltage divider rule:

$$V_b = V_{R_2} + V_{R_3} = \frac{(R_2 + R_3)E}{R_T} = \frac{(3 \Omega + 5 \Omega)(10 \text{ V})}{10 \Omega} = 8 \text{ V}$$

or $V_b = V_a - V_{ab} = E - V_{ab} = 10 \text{ V} - 2 \text{ V} = 8 \text{ V}$

- $V_c = \text{ground potential} = 0 \text{ V}$

INTERNAL RESISTANCE OF VOLTAGE SOURCES

Every source of voltage, whether a generator, battery, or laboratory supply as shown in Fig. 17(a), will have some internal resistance. The equivalent circuit of any source of voltage will therefore appear as shown in Fig. 17(b).


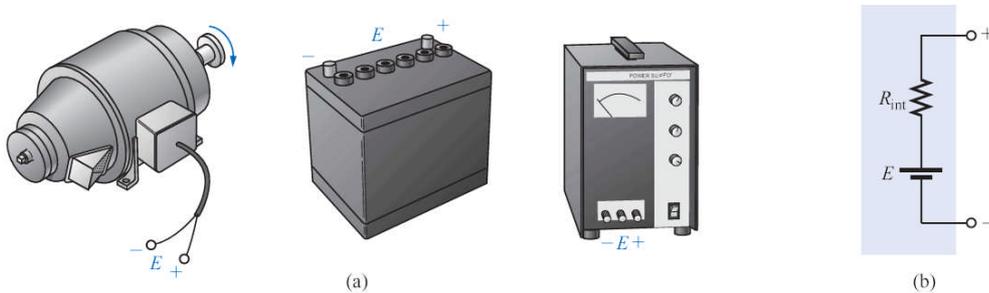


Fig (17)

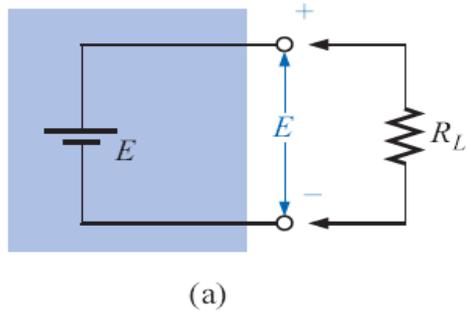
(a) Sources of dc voltage; (b) equivalent circuit.

The ideal voltage source has no internal resistance and an output voltage of E volts with no load or full load. as shown in[fig18(a)] .




Fig(18)

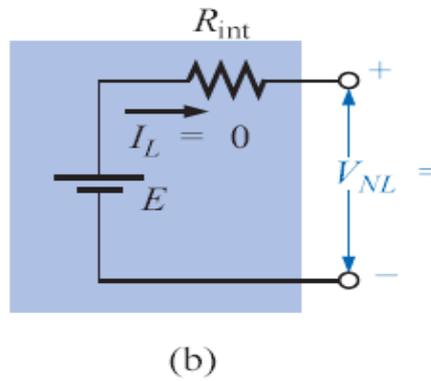In the practical case [Fig. 18(b)], where we consider the effects of the internal resistance, the output voltage will be E volts only when no-load ($I_L = 0$) conditions exist.



Fig(18)

When a load is connected [fig 18c]

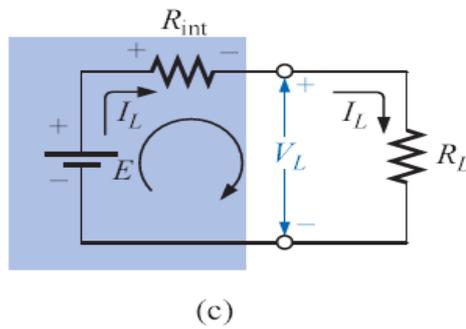

Fig(18)

By applying Kirchhoff's voltage law around the indicated loop of Fig18(c), we obtain:

$$E - I_L R_{\text{int}} - V_L = 0$$

or, since

$$E = V_{NL}$$

we have

$$V_{NL} - I_L R_{\text{int}} - V_L = 0$$

and


$$V_L = V_{NL} - I_L R_{\text{int}}$$

$$R_{\text{int}} = \frac{V_{NL} - V_L}{I_L} = \frac{V_{NL}}{I_L} - \frac{I_L R_L}{I_L}$$

and

$$R_{\text{int}} = \frac{V_{NL}}{I_L} - R_L$$

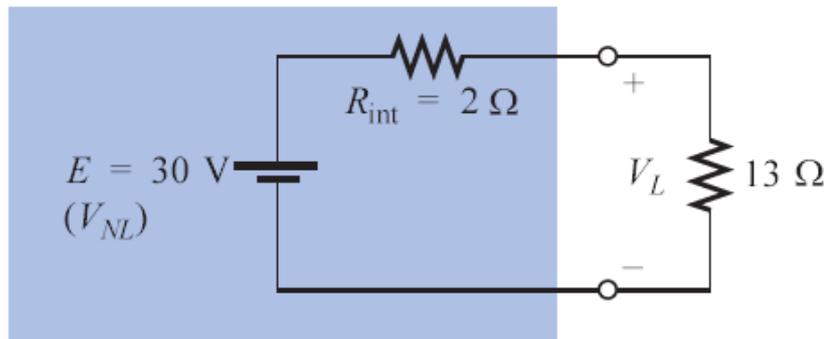EXAMPLE 9 The battery of Fig. (19) has an internal resistance of 2Ω . Find the voltage V_L and the power lost to the internal resistance if the applied load is a 13Ω resistor.



Fig(19)

Solution:

$$I_L = \frac{30 \text{ V}}{2 \Omega + 13 \Omega} = \frac{30 \text{ V}}{15 \Omega} = 2 \text{ A}$$

$$V_L = V_{NL} - I_L R_{\text{int}} = 30 \text{ V} - (2 \text{ A})(2 \Omega)$$

$$P_{\text{lost}} = I_L^2 R_{\text{int}} = (2 \text{ A})^2 (2 \Omega) = (4)(2) = 8$$